

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Click to edit Master title style

5. RLC CIRCUITS & RESONANCE

DT008/2: Circuits & Devices 2 (ELTR-2001)

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Series RLC Circuits

DT008/2: Circuits & Devices 2 (ELTR-2001)

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING


Series RLC circuits

When a circuit contains an inductor and capacitor in series, the reactance of each tend to cancel.

The total reactance is given by $X_{tot} = |X_L - X_C|$

The total impedance is given by $Z_{tot} = \sqrt{R^2 + X_{tot}^2}$

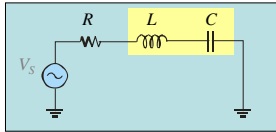The phase angle is given by $\theta = \tan^{-1}\left(\frac{X_{tot}}{R}\right)$



DT008/2: Circuits & Devices 2 (ELTR-2001)

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Problem

1. In the circuit below, $R = 10\Omega$, $L = 5\text{mH}$, $C = 0.047\mu\text{F}$. Determine the impedance and phase angle. What is the total reactance?

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(5\text{ kHz})(0.047\mu\text{F})} = 677\Omega$$


$$X_L = 2\pi fL = 2\pi(5\text{ kHz})(5\text{ mH}) = 157\Omega$$

$$Z = \sqrt{R^2 + (X_C - X_L)^2} = \sqrt{(10\Omega)^2 + (677\Omega - 157\Omega)^2} = \sqrt{(10\Omega)^2 + (520\Omega)^2} = 520\Omega$$

$$\theta = \tan^{-1}\left(\frac{X_C - X_L}{R}\right) = \tan^{-1}\left(\frac{520\Omega}{10\Omega}\right) = 88.9^\circ \text{ (V, lagging I)}$$

$$X_{tot} = X_C - X_L = 520\Omega \text{ Capacitive}$$

$X_C > X_L \dots \text{capacitive}$

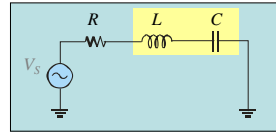

DT008/2: Circuits & Devices 2 (ELTR-2001)

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Variation of X_L and X_C with frequency

In a series RLC circuit, the circuit can be capacitive or inductive, depending on the frequency.

$$X_C = \frac{1}{2\pi fC}$$

$$X_L = 2\pi fL$$

At the frequency where $X_C = X_L$, the circuit is at series resonance.

Below the resonant frequency, the circuit is predominantly capacitive.

Above the resonant frequency, the circuit is predominantly inductive.

DT0082: Circuits & Devices 2 (ELTR-2001) 5

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Impedance of series RLC circuits

Example-1 What is the total impedance and phase angle of the series RLC circuit if $R = 1.0 \text{ k}\Omega$, $X_L = 2.0 \text{ k}\Omega$, and $X_C = 5.0 \text{ k}\Omega$?

The total reactance is $X_{\text{tot}} = |X_L - X_C| = |2.0 \text{ k}\Omega - 5.0 \text{ k}\Omega| = 3.0 \text{ k}\Omega$

The total impedance is $Z_{\text{tot}} = \sqrt{R^2 + X_{\text{tot}}^2} = \sqrt{1.0 \text{ k}\Omega^2 + 3.0 \text{ k}\Omega^2} = 3.16 \text{ k}\Omega$

The phase angle is $\theta = \tan^{-1}\left(\frac{X_{\text{tot}}}{R}\right) = \tan^{-1}\left(\frac{3.0 \text{ k}\Omega}{1.0 \text{ k}\Omega}\right) = 71.6^\circ$

The circuit is capacitive, so I leads V by 71.6° .

DT0082: Circuits & Devices 2 (ELTR-2001) 6

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Impedance of series RLC circuits

Example-2 What is the magnitude of the impedance for the circuit?

$$X_L = 2\pi fL = 2\pi(100 \text{ kHz})(330 \mu\text{H}) = 207 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(100 \text{ kHz})(2000 \text{ pF})} = 796 \Omega$$

$$X_{\text{tot}} = |X_L - X_C| = |207 \Omega - 796 \Omega| = 589 \Omega$$

$$Z = \sqrt{(470 \Omega)^2 + (589 \Omega)^2} = 753 \Omega$$

DT0082: Circuits & Devices 2 (ELTR-2001) 7

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Impedance of series RLC circuits

Depending on the frequency, the circuit can appear to be capacitive or inductive.

The circuit in Example-2 was capacitive because $X_C > X_L$.

DT0082: Circuits & Devices 2 (ELTR-2001) 8

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Impedance of series RLC circuits

Example-3 What is the total impedance for the circuit when the frequency is increased to 400 Hz?


$$X_L = 2\pi fL = 2\pi(400 \text{ kHz})(330 \mu\text{H}) = 829 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(400 \text{ kHz})(2000 \text{ pF})} = 199 \Omega$$

$$X_{\text{tot}} = |X_L - X_C| = |829 \Omega - 199 \Omega| = 630 \Omega$$

$$Z = \sqrt{(470 \Omega)^2 + (630 \Omega)^2} = 786 \Omega$$

The circuit is now inductive.

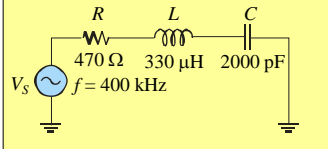


DT008/2: Circuits & Devices 2 (ELTR-2001) 9

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Impedance of series RLC circuits

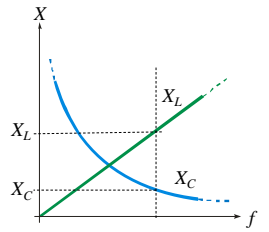By changing the frequency, the circuit in Example-3 is now inductive because $X_L > X_C$




DT008/2: Circuits & Devices 2 (ELTR-2001) 10

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Voltages in a series RLC circuits

The voltages across the *RLC* components must add to the source voltage in accordance with KVL. Because of the opposite phase shift due to *L* and *C*, V_L and V_C effectively subtract.

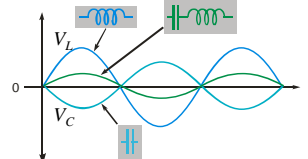Notice that V_C is out of phase with V_L . When they are algebraically added, the result is....




This example is inductive.

DT008/2: Circuits & Devices 2 (ELTR-2001) 11

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Series resonance

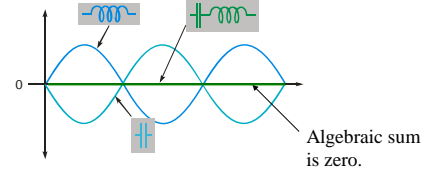At series resonance, X_C and X_L cancel. V_C and V_L also cancel because the voltages are equal and opposite. The circuit is purely resistive at resonance.



Algebraic sum is zero.

DT008/2: Circuits & Devices 2 (ELTR-2001) 12

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Resonance Frequency


The formula for resonance can be found by setting $X_C = X_L$.
The result is

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

Example What is the resonant frequency for the circuit?

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{(330\ \mu\text{H})(2000\ \text{pF})}}$$

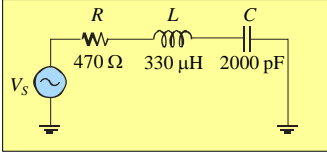
$$= 196\ \text{kHz}$$


DT008/2: Circuits & Devices 2 (ELTR-2001) 13

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING


Series resonance

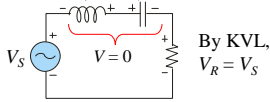Ideally, at resonance the sum of V_L and V_C is zero.



By KVL,
 $V_R = V_S$

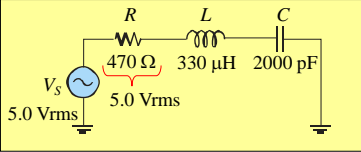Example What is V_R at resonance?
5.0 Vrms




DT008/2: Circuits & Devices 2 (ELTR-2001) 14

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Impedance of series RLC circuits

The general shape of the impedance versus frequency for a series RLC circuit is superimposed on the curves for X_L and X_C .

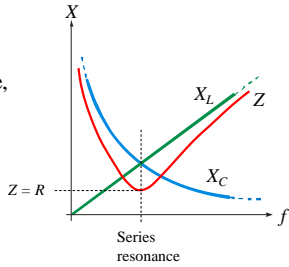Notice that at the resonant frequency, the circuit is resistive, and $Z = R$.



DT008/2: Circuits & Devices 2 (ELTR-2001) 15

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Series resonance

Summary of important concepts for series resonance:

- Capacitive and inductive reactances are equal.
- Total impedance is a minimum and is resistive.
- The current is maximum.
- The phase angle between V_S and I_S is zero.
- f_r is given by $f_r = \frac{1}{2\pi\sqrt{LC}}$



DT008/2: Circuits & Devices 2 (ELTR-2001) 16

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Series resonant filters (band-pass)

An application of series resonant circuits is in filters.
A band-pass filter allows signals within a range of frequencies to pass.


Circuit response:

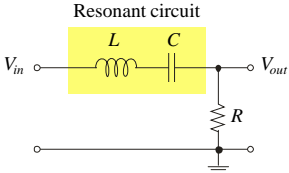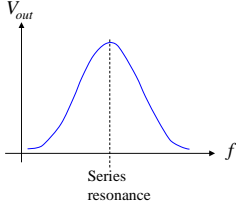DT0802: Circuits & Devices 2 (ELTR-2001) **17**


SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

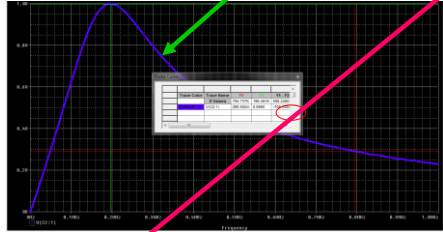RLC Series resonant filters PSPICE – Voltage o/p and Current



$$f_r = \frac{1}{2\pi\sqrt{LC}}$$


$$= \frac{1}{2\pi\sqrt{(330\ \mu\text{H})(2000\ \text{pF})}}$$
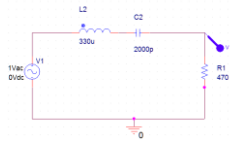
$$= 196\ \text{kHz}$$


DT0802: Circuits & Devices 2 (ELTR-2001) **18**

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

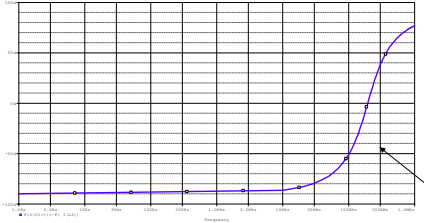RLC Series resonant filters PSPICE – Phase difference between Voltage source and Current




$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{(330\ \mu\text{H})(2000\ \text{pF})}}$$

$$= 196\ \text{kHz}$$

Phase difference = 0 at resonance



DT0802: Circuits & Devices 2 (ELTR-2001) **19**


SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Series resonant filters (band width)

The response has a peak because at the *series* resonant frequency, the current is maximum at resonance and falls off before and after resonance. This develops the maximum voltage across the resistor at resonance.

The bandwidth (BW) of the filter is the range of frequencies for which the output is equal to or greater than 70.7% of the maximum value.

f_1 and f_2 are commonly referred to as the *critical frequencies*, *cutoff frequencies* or *half-power frequencies*.

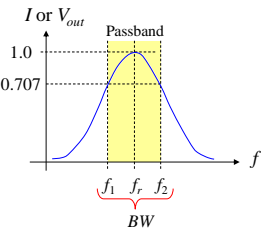

DT0802: Circuits & Devices 2 (ELTR-2001) **20**

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Decibels

Filter responses are often given in terms of decibels, which is defined as

$$\text{dB} = 10 \log \left(\frac{P_{\text{out}}}{P_{\text{in}}} \right)$$

Because it is a ratio, the decibel is dimensionless. One of the most important decibel ratios occurs when the power ratio is 1:2. This is called the -3 dB frequency, because

$$\text{dB} = 10 \log \left(\frac{1}{2} \right) = -3 \text{ dB}$$

Another useful definition for the decibel, when measuring voltages across the same impedance is

$$\text{dB} = 20 \log \left(\frac{V_{\text{out}}}{V_{\text{in}}} \right)$$

DT008/2: Circuits & Devices 2 (ELTR-2001) **21**

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Selectivity

Selectivity describes the basic frequency response of a resonant circuit. (The -3 dB frequencies are marked by the dots.)

The bandwidth is inversely proportional to Quality Factor Q in accordance with the formula, $BW = \frac{f_r}{Q}$

Question
Which curve represents the highest Q ? The one with the greatest selectivity.

DT008/2: Circuits & Devices 2 (ELTR-2001) **22**

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Series resonant filters (band-stop)

By taking the output across the resonant circuit, a band-stop (or notch) filter is produced.

Series resonant filters

Circuit response:

DT008/2: Circuits & Devices 2 (ELTR-2001) **23**

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Notch filter or band reject filter

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{(330 \mu\text{H})(2000 \text{ pF})}}$$

$$= 196 \text{ kHz}$$

DT008/2: Circuits & Devices 2 (ELTR-2001) **24**

Parallel RLC Circuits

DT0802: Circuits & Devices 2 (ELTR-2001)


25

Parallel RLC Circuit

- The **Parallel** RLC Circuit is the exact opposite to the series circuit we looked at in the previous, although some of the previous concepts and equations still apply.

In the parallel RLC circuit, the supply voltage, V_s is common to all three components, whilst the supply current I_s consists of three parts.

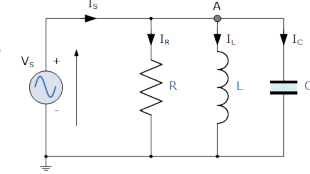The current flowing through the resistor, I_R , the current flowing through the inductor, I_L and the current through the capacitor, I_C .



Like the series RLC circuit, we can solve this circuit using the phasor or vector method but this time the vector diagram will have the **voltage as its reference** with the three current vectors plotted with respect to the voltage.

The phasor diagram for a parallel RLC circuit is produced by combining together the three individual phasors for each component and adding the currents vectorially.

DT0802: Circuits & Devices 2 (ELTR-2001)


26

Phasor Diagram for Parallel RLC Circuit

Since the voltage across the circuit is common to all three circuit elements we can use this as the reference vector with the three current vectors drawn relative to this at their corresponding angles.

The resulting vector I_s is obtained by adding together two of the vectors, I_L and I_C and then adding this sum to the remaining vector I_R .

The resulting angle obtained between V and I_s will be the circuits phase angle as shown below.

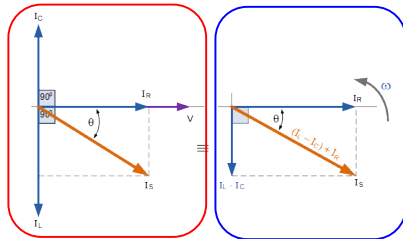

DT0802: Circuits & Devices 2 (ELTR-2001)


27

Phasor Diagram for Parallel RLC Circuit

Since the voltage across the circuit is common to all three circuit elements we can use this as the reference vector with the three current vectors drawn relative to this at their corresponding angles.

The resulting vector I_s is obtained by adding together two of the vectors, I_L and I_C and then adding this sum to the remaining vector I_R .

The resulting angle obtained between V and I_s will be the circuits phase angle as shown below.

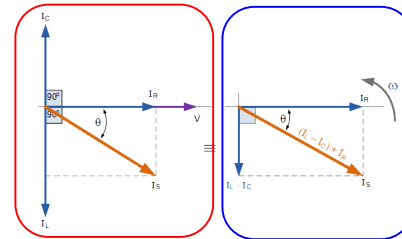

DT0802: Circuits & Devices 2 (ELTR-2001)

28

Current Triangle for a Parallel RLC

$$I_S^2 = I_R^2 + (I_L - I_C)^2$$

$$I_S = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$\therefore I_S = \sqrt{\left(\frac{V}{R}\right)^2 + \left(\frac{V}{X_L} - \frac{V}{X_C}\right)^2} = \frac{V}{Z}$$

where: $I_R = \frac{V}{R}$, $I_L = \frac{V}{X_L}$, $I_C = \frac{V}{X_C}$

DT008/2: Circuits & Devices 2 (ELTR-2001) 29

Impedance of a Parallel RLC Circuit

- the final equation for a parallel RLC circuit produces complex impedance's for each parallel branch as each element becomes the reciprocal of impedance, ($1/Z$) with the reciprocal of impedance being called Admittance.

In parallel AC circuits it is more convenient to use admittance, symbol (Y) to solve complex branch impedance's especially when two or more parallel branch impedance's are involved (helps with the math's).

The total admittance of the circuit can simply be found by the addition of the parallel admittances.

Then the total impedance, Z_T of the circuit will therefore be $1/Y_T$ Siemens as shown.

$$R = \frac{V}{I_R} \quad X_L = \frac{V}{I_L} \quad X_C = \frac{V}{I_C}$$

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}}$$


$$\therefore \frac{1}{Z} = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}$$

DT008/2: Circuits & Devices 2 (ELTR-2001) 30

Admittance of a Parallel RLC Circuit

- The new unit for admittance is the Siemens, abbreviated as S , (old unit mho's Ω , ohm's in reverse).
- Admittances are added together in parallel branches, whereas impedance's are added together in series branches.

A reciprocal of impedance also a reciprocal of resistance and reactance as impedance consists of two components, R and X . Then the reciprocal of resistance is called Conductance and the reciprocal of reactance is called Susceptance.
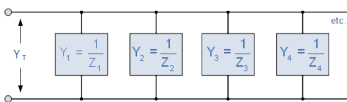
$$\frac{1}{Z_T} = Y_T = Y_1 + Y_2 + Y_3 + Y_4 + \dots \text{etc}$$


DT008/2: Circuits & Devices 2 (ELTR-2001) 31

Conductance, Admittance & Susceptance

- The units used for conductance, admittance and susceptance are all the same namely Siemens (S), which can also be thought of as the reciprocal of Ohms or ohm-1, but the symbol used for each element is different and in a pure component this is given as:

Admittance (Y):
Admittance is the reciprocal of impedance, Z and is given the symbol Y .

$$Y = \frac{1}{Z} [S]$$

Conductance (G):
Conductance is the reciprocal of resistance, R and is given the symbol G .

$$G = \frac{1}{R} [S]$$

Susceptance (B):
Susceptance is the reciprocal of a pure reactance, X and is given the symbol B .

$$B_L = \frac{1}{X_L} [S]$$

$$B_C = \frac{1}{X_C} [S]$$

DT008/2: Circuits & Devices 2 (ELTR-2001) 32

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Admittance Triangle for a Parallel RLC

- Now that we have an admittance triangle, we can use Pythagoras to calculate the magnitudes of all three sides as well as the phase angle as shown.
- from Pythagoras

$$Y = \sqrt{G^2 + (B_L - B_C)^2}$$

where: $Y = \frac{1}{Z}$ $G = \frac{1}{R}$

$$B_L = \frac{1}{\omega L} \quad B_C = \omega C$$

DT0002: Circuit 3 Devices 2 (ELTR-2001) **33**

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Admittance & Impedance

Admittance: $Y = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{\omega L} - \omega C\right)^2}$

Impedance: $Z = \frac{1}{Y} = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{\omega L} - \omega C\right)^2}}$

DT0002: Circuit 3 Devices 2 (ELTR-2001) **34**