

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Click to edit Master title style


3. CAPACITORS

DT008/2: Circuits & Devices 2 (ELTR-2001)

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

The Basic Capacitor

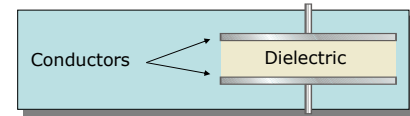Capacitors are one of the fundamental passive components. In its most basic form, it is composed of two conductive plates separated by an insulating dielectric. The ability to store charge is the definition of **capacitance**.




DT008/2: Circuits & Devices 2 (ELTR-2001)

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

The Basic Capacitor

The charging process...

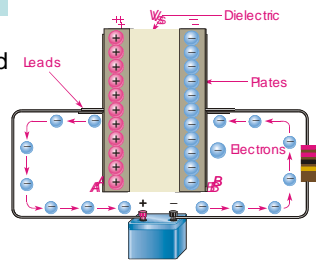Initially uncharged
Charging
Fully charged
Source removed



A capacitor with stored charge can act as a temporary battery.

DT008/2: Circuits & Devices 2 (ELTR-2001)

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitance

Capacitance is the ratio of charge to voltage

$$C = \frac{Q}{V}$$

Rearranging, the amount of charge on a capacitor is determined by the size of the capacitor (C) and the voltage (V).

$$Q = CV$$

Example If a 22 μF capacitor is connected to a 10 V source, the charge is 220 μC

DT008/2: Circuits & Devices 2 (ELTR-2001)

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitance

A capacitor stores energy in the form of an electric field that is established by the opposite charges on the two plates.
The energy of a charged capacitor is given by the equation

$$W = \frac{1}{2} CV^2$$

where

- W = the energy in joules
- C = the capacitance in farads
- V = the voltage in volts

DT008/2: Circuits & Devices 2 (ELTR-2001) 5

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitance

The capacitance of a capacitor depends on three physical characteristics.

$$C = 8.85 \times 10^{-12} \text{ F/m} \left(\frac{\epsilon_r A}{d} \right)$$

C is directly proportional to the **relative dielectric constant** and the **plate area**.
 C is inversely proportional to the **distance** between the plates

DT008/2: Circuits & Devices 2 (ELTR-2001) 6

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitance

Example Find the capacitance of a circular 4.0 cm diameter sensor immersed in oil if the plates are separated by 0.25 mm.

$$C = 8.85 \times 10^{-12} \text{ F/m} \left(\frac{\epsilon_r A}{d} \right) \quad (\epsilon_r = 4.0 \text{ for oil})$$

The plate area is $A = \pi r^2 = \pi (0.02 \text{ m})^2 = 1.26 \times 10^{-3} \text{ m}^2$
The distance between the plates is $0.25 \times 10^{-3} \text{ m}$


$$C = 8.85 \times 10^{-12} \text{ F/m} \left(\frac{(4.0)(1.26 \times 10^{-3} \text{ m}^2)}{0.25 \times 10^{-3} \text{ m}} \right) = 178 \text{ pF}$$

DT008/2: Circuits & Devices 2 (ELTR-2001) 7

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitor types

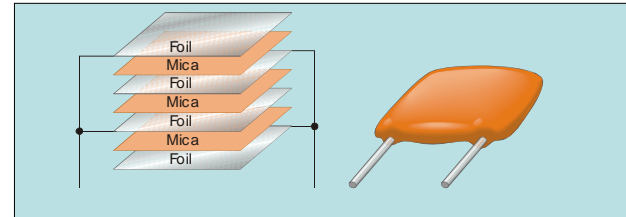Mica
Mica capacitors are small with high working voltage.
The **working voltage** is the voltage limit that cannot be exceeded.



The diagram illustrates the internal structure of a mica capacitor, showing alternating layers of foil and mica dielectric. To the right, a photograph shows a small, orange, oval-shaped mica capacitor with two leads.


DT008/2: Circuits & Devices 2 (ELTR-2001) 8

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitor types

Ceramic disk

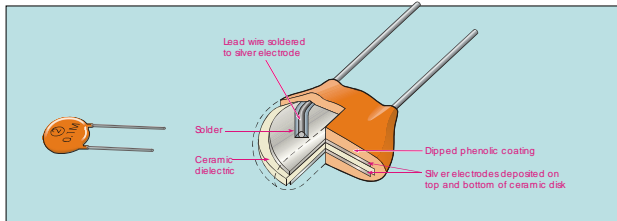Ceramic disks are small nonpolarized capacitors. They have relatively high capacitance due to high ϵ_r .



The diagram shows a cross-section of a ceramic disk capacitor. It features a central lead wire soldered to a silver electrode. The capacitor is coated with a dipped phenolic coating. The internal structure shows silver electrodes deposited on the top and bottom of the ceramic disk, which is made of a ceramic dielectric.


DT008/2: Circuits & Devices 2 (ELTR-2001) 9

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitor types

Plastic Film

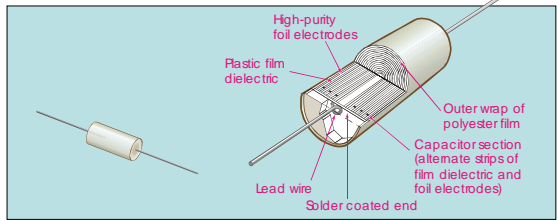Plastic film capacitors are small and nonpolarized. They have relatively high capacitance due to larger plate area.



The diagram shows a cross-section of a plastic film capacitor. It features high-purity foil electrodes and a plastic film dielectric. The capacitor is wrapped in an outer wrap of polyester film. The internal structure shows alternate strips of film dielectric and foil electrodes. The lead wire is solder coated at the end.


DT008/2: Circuits & Devices 2 (ELTR-2001) 10

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitor types

Electrolytic (two types)

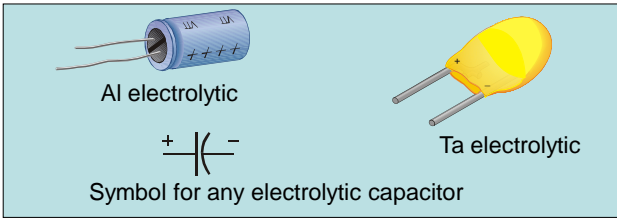Electrolytic capacitors have very high capacitance but they are not as precise as other types and tend to have more leakage current. Electrolytic types are polarized.



The diagram shows two types of electrolytic capacitors: an Al electrolytic (aluminum) and a Ta electrolytic (tantalum). The Al electrolytic is shown as a blue cylindrical component with two leads. The Ta electrolytic is shown as a yellow cylindrical component with two leads. The symbol for any electrolytic capacitor is shown as a capacitor symbol with a '+' sign on the left and a '-' sign on the right.


DT008/2: Circuits & Devices 2 (ELTR-2001) 11

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitor types: Variable

Variable

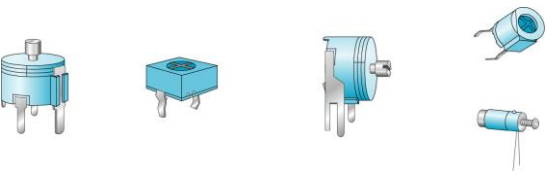Variable capacitors typically have small capacitance values and are usually adjusted manually. A solid-state device that is used as a variable capacitor is the varactor diode; it is adjusted with an electrical signal.



The diagram shows four different types of variable capacitors: a large blue cylindrical component, a small blue square component, a blue cylindrical component with a central adjustment screw, and a small blue cylindrical component with two leads.


DT008/2: Circuits & Devices 2 (ELTR-2001) 12

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitor labeling

Capacitors use several labeling methods. Small capacitors values are frequently stamped on them such as .001 or .01, which have implied units of microfarads.

Electrolytic capacitors have larger values, so are read as μF . The unit is usually stamped as μF , but some older ones may be shown as MF or MMF).

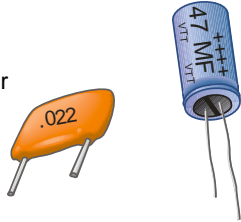

DT0002: Circuits & Devices 2 (ELTR-2001) 13


SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitor labeling

A label such as 103 or 104 is read as 10×10^3 (10,000 pF) or 10×10^4 (100,000 pF) respectively. (Third digit is the multiplier.)

When values are marked as 330 or 6800, the units are picofarads.

Example



What is the value of each capacitor? Both are 2200 pF.

DT0002: Circuits & Devices 2 (ELTR-2001) 14

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Problem

(a) What quantity of electric charge will produce a p.d. of 200 V between the plates of a capacitor of 5 F?

(b) Compare the magnitude of two capacitors, one having two circular plates of diameter 40 mm and placed 0.5 mm apart, the other having two square plates of side 50 mm and placed 0.75 mm apart. It may be assumed that the same dielectric material is used between the plates in each case.

[1 mC, 1.33]

DT0002: Circuits & Devices 2 (ELTR-2001) 15

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Series capacitors

When capacitors are connected in series, the total capacitance is smaller than the smallest one.

The general equation for capacitors in series is

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_T}}$$

The total capacitance of two capacitors is

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

...or you can use the product-over-sum rule


$$C_T = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

DT0002: Circuits & Devices 2 (ELTR-2001) 16

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Series capacitors

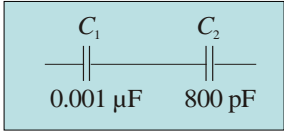Example If a $0.001 \mu\text{F}$ capacitor is connected in series with an 800 pF capacitor, the total capacitance is 444 pF



DT008/2: Circuits & Devices 2 (ELTR-2001) 17

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING


Parallel capacitors

When capacitors are connected in parallel, the total capacitance is the sum of the individual capacitors.

The general equation for capacitors in parallel is

$$C_T = C_1 + C_2 + C_3 + \dots C_n$$

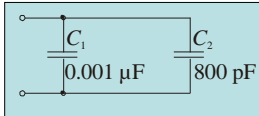Example If a $0.001 \mu\text{F}$ capacitor is connected in parallel with an 800 pF capacitor, the total capacitance is 1800 pF



DT008/2: Circuits & Devices 2 (ELTR-2001) 18

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitive reactance

Capacitive reactance is the opposition to ac by a capacitor. The equation for capacitive reactance is

$$X_c = \frac{1}{2\pi fC}$$

Example The reactance of a $0.047 \mu\text{F}$ capacitor when a frequency of 15 kHz is applied is 226Ω

DT008/2: Circuits & Devices 2 (ELTR-2001) 19

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitive reactance : Series

When capacitors are in series, the total reactance is the sum of the individual reactances. That is,

$$X_{C(\text{tot})} = X_{C1} + X_{C2} + X_{C3} + \dots + X_{Cn}$$

Example Assume three $0.033 \mu\text{F}$ capacitors are in series with a 2.5 kHz ac source. What is the total reactance?

Solution: The reactance of each capacitor is

$$X_c = \frac{1}{2\pi fC} = \frac{1}{2\pi(2.5 \text{ kHz})(0.033 \mu\text{F})} = 1.93 \text{ k}\Omega$$

$$X_{C(\text{tot})} = X_{C1} + X_{C2} + X_{C3} = 1.93 \text{ k}\Omega + 1.93 \text{ k}\Omega + 1.93 \text{ k}\Omega = 5.79 \text{ k}\Omega$$

DT008/2: Circuits & Devices 2 (ELTR-2001) 20

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitive reactance: Parallel

When capacitors are in parallel, the total reactance is the reciprocal of the sum of the reciprocals of the individual reactances. That is,

$$X_{C(\text{tot})} = \frac{1}{\frac{1}{X_{C1}} + \frac{1}{X_{C2}} + \frac{1}{X_{C3}} + \dots + \frac{1}{X_{Cn}}}$$

Example If the three 0.033 μF capacitors from the last example are placed in parallel with the 2.5 kHz ac source, what is the total reactance?

Solution: The reactance of each capacitor is 1.93 k Ω

$$X_{C(\text{tot})} = \frac{1}{\frac{1}{X_{C1}} + \frac{1}{X_{C2}} + \frac{1}{X_{C3}}} = \frac{1}{\frac{1}{1.93 \text{ k}\Omega} + \frac{1}{1.93 \text{ k}\Omega} + \frac{1}{1.93 \text{ k}\Omega}} = 643 \Omega$$

DT008/2: Circuits & Devices 2 (ELTR-2001) 21

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitive Voltage Divider

Two capacitors in series are commonly used as a capacitive voltage divider. The capacitors split the output voltage in proportion to their reactance (and inversely proportional to their capacitance).


Example What is the output voltage for the capacitive voltage divider?

Solution:

$$X_{C1} = \frac{1}{2\pi f C_1} = \frac{1}{2\pi(33 \text{ kHz})(1000 \text{ pF})} = 4.82 \text{ k}\Omega$$

$$X_{C2} = \frac{1}{2\pi f C_2} = \frac{1}{2\pi(33 \text{ kHz})(0.01 \mu\text{F})} = 482 \Omega$$

$$X_{C(\text{tot})} = X_{C1} + X_{C2} = 4.82 \text{ k}\Omega + 482 \Omega = 5.30 \text{ k}\Omega$$
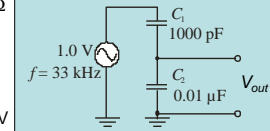
$$V_{\text{out}} = \left(\frac{X_{C2}}{X_{C(\text{tot})}} \right) V_s = \left(\frac{482 \Omega}{5.30 \text{ k}\Omega} \right) 1.0 \text{ V} = 91 \text{ mV}$$


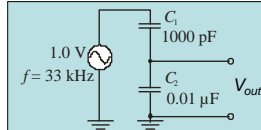
DT008/2: Circuits & Devices 2 (ELTR-2001) 22

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Capacitive Voltage Divider

Instead of using a ratio of reactances in the capacitor voltage divider equation, you can use a ratio of the total series capacitance to the output capacitance (multiplied by the input voltage). The result is the same. For the problem presented in the last slide,

$$C_{\text{tot}} = \frac{C_1 C_2}{C_1 + C_2} = \frac{(1000 \text{ pF})(0.01 \mu\text{F})}{1000 \text{ pF} + 0.01 \mu\text{F}} = 909 \text{ pF}$$

$$V_{\text{out}} = \left(\frac{C_{\text{tot}}}{C_2} \right) V_s = \left(\frac{909 \text{ pF}}{0.01 \mu\text{F}} \right) 1.0 \text{ V} = 91 \text{ mV}$$


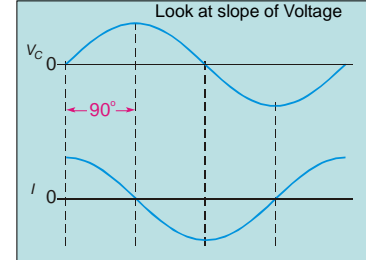
DT008/2: Circuits & Devices 2 (ELTR-2001) 23

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING





Capacitive phase shift




$$I = \frac{Q}{t} \quad i = \frac{dQ}{dt} = C \frac{dV}{dt} = C \frac{d(V_0 \sin(t))}{dt} = CV_0 \cos(t)$$

When a sine wave is applied to a capacitor, there is a phase shift between voltage and current such that current always leads the voltage by 90°.



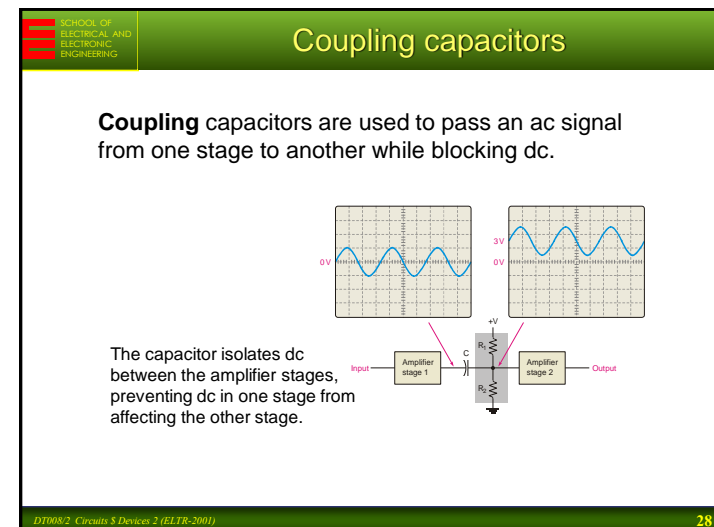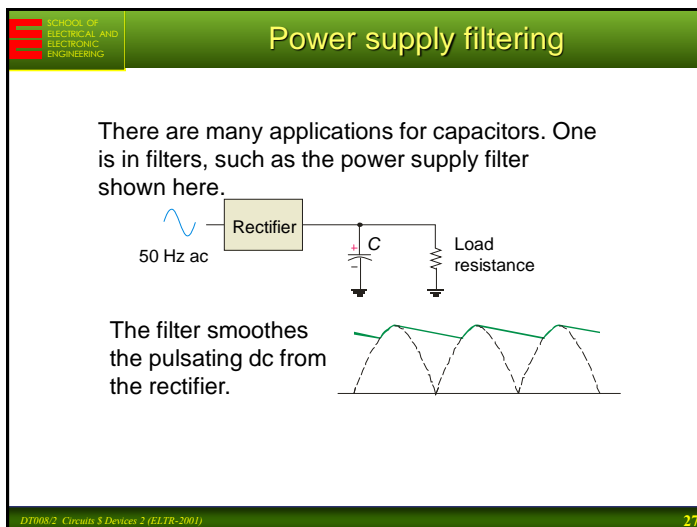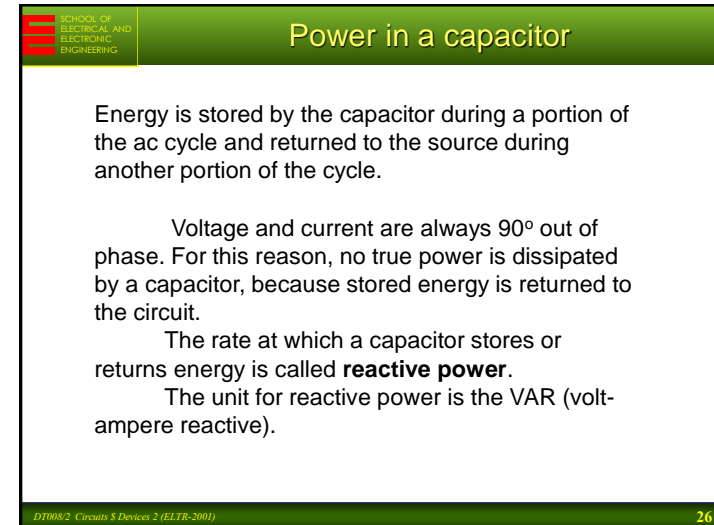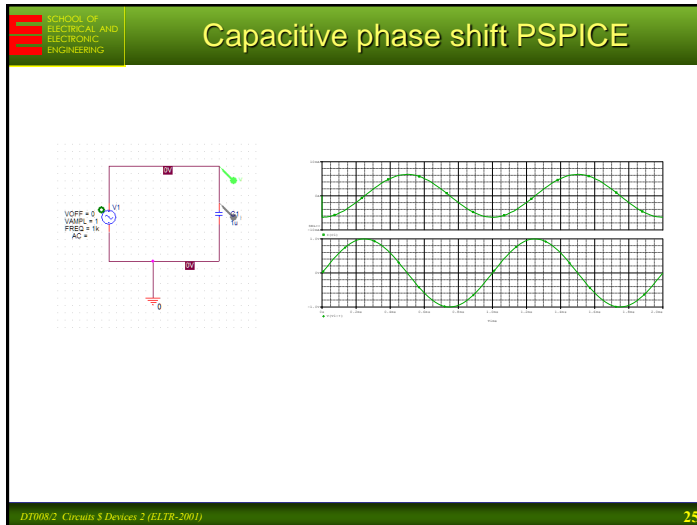DT008/2: Circuits & Devices 2 (ELTR-2001) 24



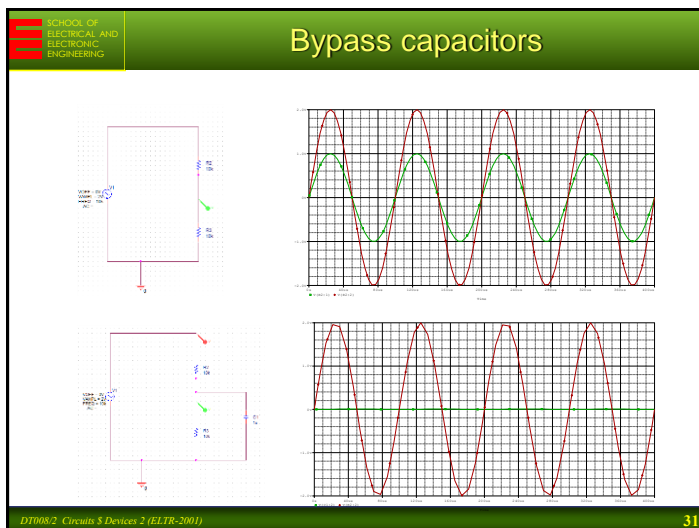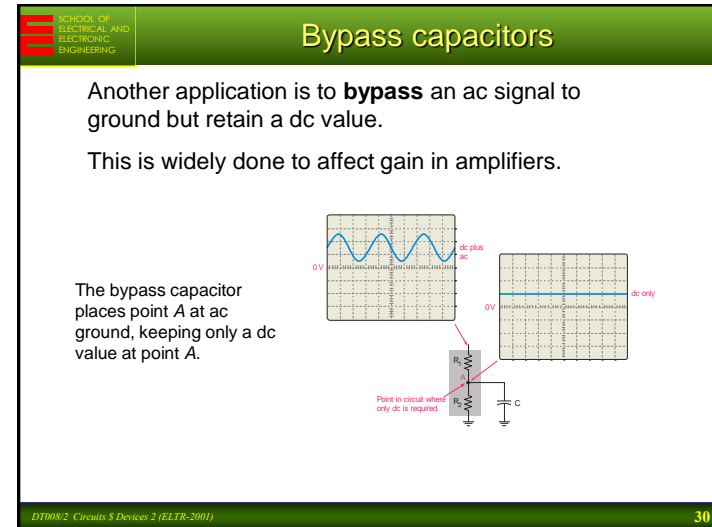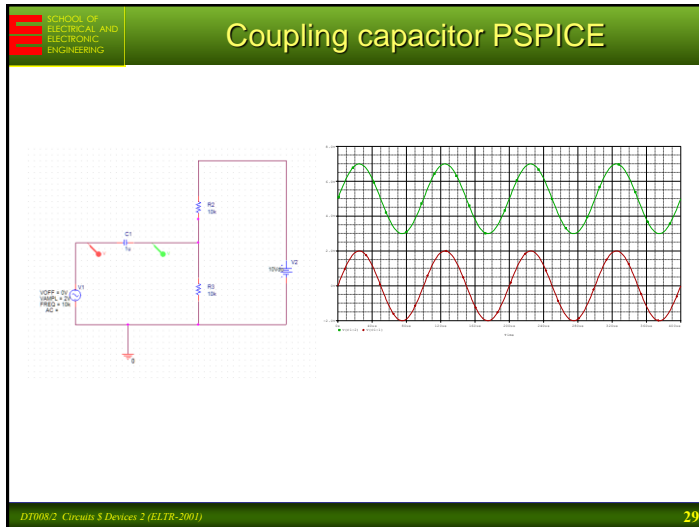

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING


The Basic Inductor

When a length of wire is formed into a coil, it becomes a basic inductor. When there is current in the inductor, a three-dimensional magnetic field is created.

A change in current causes the magnetic field to change.

This in turn induces a voltage across the inductor that opposes the original change in current.

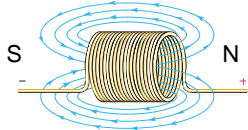An inductor stores energy in the magnetic field created by the current.



$$W = \frac{1}{2} LI^2$$

DT0002: Circuits & Devices 2 (ELTR-2001)


33

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

The Basic Inductor

One henry is the inductance of a coil when a current, changing at a rate of one ampere per second, induces one volt across the coil. Most coils are much smaller than 1 H.

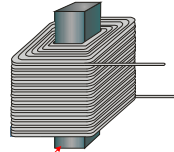The effect of inductance is greatly magnified by adding turns and winding them on a magnetic material. Large inductors and transformers are wound on a core to increase the inductance.



Magnetic core

DT0002: Circuits & Devices 2 (ELTR-2001)


34

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Faraday's law

Faraday's law was introduced in Chapter 7 and repeated here because of its importance to inductors.

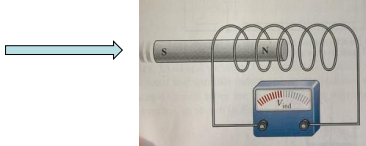The amount of voltage induced in a coil is directly proportional to the rate of change of the magnetic field with respect to the coil.



Move magnet faster => more voltage

DT0002: Circuits & Devices 2 (ELTR-2001)

35

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Lenz's law

When the current through a coil changes and an induced voltage is created as a result of the changing magnetic field, the direction of the induced voltage is such that it always opposes the change in the current.

DT0002: Circuits & Devices 2 (ELTR-2001)

36


SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Lenz's law

When the current through a coil changes and an induced voltage is created as a result of the changing magnetic field, the direction of the induced voltage is such that it always opposes the change in the current.

A basic circuit to demonstrate Lenz's law is shown.

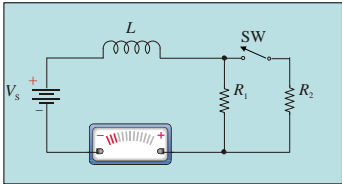Initially, the SW is open and there is a small current in the circuit through L and R_1 .




DT008/2: Circuits & Devices 2 (ELTR-2001)

37

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Lenz's law

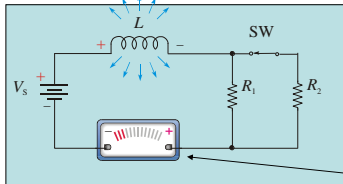SW closes and immediately a voltage appears across L that tends to oppose any *change* in current.



Initially, the meter reads same current as before the switch was closed.


DT008/2: Circuits & Devices 2 (ELTR-2001)

38

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Lenz's law

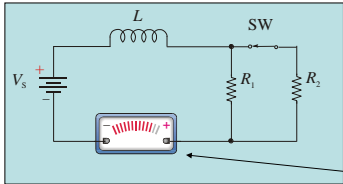After a time, the current stabilizes at a higher level (due to I_2) as the voltage decays across the coil.



Later, the meter reads a higher current because of the load change.


DT008/2: Circuits & Devices 2 (ELTR-2001)

39

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Inductor Circuit PSpice

Current

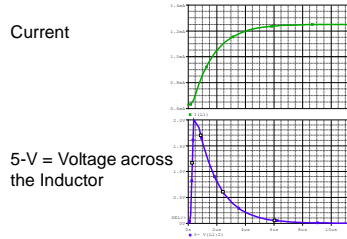

5-V = Voltage across the Inductor

DT008/2: Circuits & Devices 2 (ELTR-2001)


40

Practical inductors

In addition to inductance, actual inductors have winding resistance (R_w) due to the resistance of the wire and winding capacitance (C_w) between turns.

An equivalent circuit for a practical inductor including these effects is shown:

Notice that the winding resistance is in series with the coil and the winding capacitance is in parallel with both.

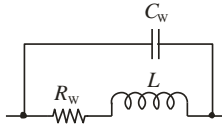


DT0082: Circuits & Devices 2 (ELTR-2001) **41**

Types of inductors

There are a variety of inductors, depending on the amount of inductance required and the application.

Some, with fine wires, are encapsulated and may appear like a resistor.

Common symbols for inductors (coils) are

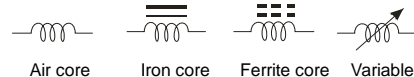

Air core Iron core Ferrite core Variable

DT0082: Circuits & Devices 2 (ELTR-2001) **42**

Factors affecting inductance

Four factors affect the amount of inductance for a coil.

The equation for the inductance of a coil is

$$L = \frac{N^2 \mu A}{l}$$

where


- L = inductance in Henries
- N = number of turns of wire
- μ = permeability in H/m (same as Wb/At-m)
- l = coil length on meters

DT0082: Circuits & Devices 2 (ELTR-2001) **43**

Inductance calculation

Example What is the inductance of a 2 cm long, 150 turn coil wrapped on an low carbon steel core that is 0.5 cm diameter?

The permeability of low carbon steel is 2.5×10^{-4} H/m

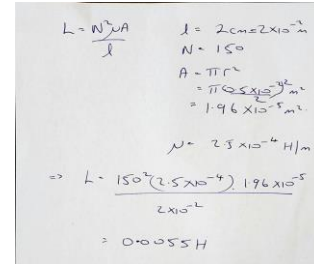


DT0082: Circuits & Devices 2 (ELTR-2001) **44**

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Practical inductors

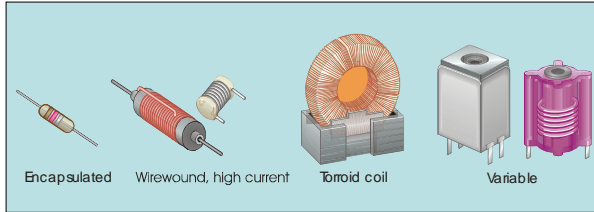Inductors come in a variety of sizes.
A few common ones are shown here.



Encapsulated Wirewound, high current Toroid coil Variable

DT008/2: Circuits & Devices 2 (ELTR-2001) 45

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Series inductors


When inductors are connected in series, the total inductance is the sum of the individual inductors. The general equation for inductors in series is

$$L_T = L_1 + L_2 + L_3 + \dots L_n$$

Example

If a 1.5 mH inductor is connected in series with an 680 μ H inductor, the total inductance is

2.18 mH

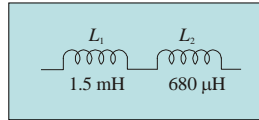

DT008/2: Circuits & Devices 2 (ELTR-2001) 46

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Parallel inductors

When inductors are connected in parallel, the total inductance is smaller than the smallest one.

The general equation for inductors in parallel is

$$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_n}}$$

The total inductance of two inductors is

$$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$

...or you can use the product-over-sum rule.

$$L_T = \frac{L_1 \cdot L_2}{L_1 + L_2}$$

DT008/2: Circuits & Devices 2 (ELTR-2001) 47


SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Parallel inductors

Example

If a 1.5 mH inductor is connected in parallel with an 680 μ H inductor, the total inductance is

468 μ H

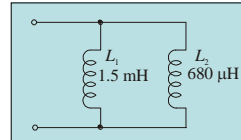

DT008/2: Circuits & Devices 2 (ELTR-2001) 48

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Inductive reactance

Inductive reactance is the opposition to ac by an inductor.

The equation for inductive reactance is

Example $X_L = 2\pi fL$

The reactance of a 33 μH inductor when a frequency of 550 kHz is applied is 114 Ω

DT0002: Circuits & Devices 2 (ELTR-2001) 49

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Inductive reactance : Series

When inductors are in series, the total reactance is the sum of the individual reactances. That is,

$$X_{L(\text{tot})} = X_{L1} + X_{L2} + X_{L3} + \dots + X_{Ln}$$

Example Assume three 220 μH inductors are in series with a 455 kHz ac source. What is the total reactance?

Solution: The reactance of each inductor is

$$X_L = 2\pi fL = 2\pi (455 \text{ kHz})(220 \mu\text{H}) = 629 \Omega$$

$$X_{L(\text{tot})} = X_{L1} + X_{L2} + X_{L3}$$

$$= 629 \Omega + 629 \Omega + 629 \Omega = 1.89 \text{ k}\Omega$$

DT0002: Circuits & Devices 2 (ELTR-2001) 50

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Inductive reactance: Parallel

When inductors are in parallel, the total reactance is the reciprocal of the sum of the reciprocals of the individual reactances. That is,

$$X_{L(\text{tot})} = \frac{1}{\frac{1}{X_{L1}} + \frac{1}{X_{L2}} + \frac{1}{X_{L3}} + \dots + \frac{1}{X_{Ln}}}$$

Example If the three 220 μH inductors from the last example are placed in parallel with the 455 kHz ac source, what is the total reactance?

Solution: The reactance of each inductor is 629 Ω


$$X_{L(\text{tot})} = \frac{1}{\frac{1}{X_{L1}} + \frac{1}{X_{L2}} + \frac{1}{X_{L3}}} = \frac{1}{\frac{1}{629 \Omega} + \frac{1}{629 \Omega} + \frac{1}{629 \Omega}} = 210 \Omega$$

DT0002: Circuits & Devices 2 (ELTR-2001) 51

SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING

Inductive phase shift

When a sine wave is applied to an inductor, there is a phase shift between voltage and current such that voltage always leads the current by 90°.

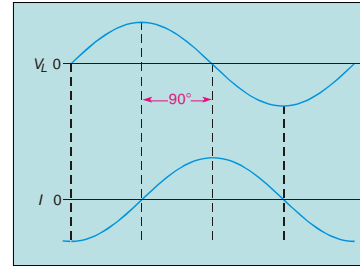

DT0002: Circuits & Devices 2 (ELTR-2001) 52

SCHOOL OF
ELECTRICAL AND
ELECTRONIC
ENGINEERING

Power in an inductor

True Power: Ideally, inductors do not dissipate power. However, a small amount of power is dissipated in winding resistance given by the equation:

$$P_{\text{true}} = (I_{\text{rms}})^2 R_W$$

Reactive Power: Reactive power is a measure of the rate at which the inductor stores and returns energy. One form of the reactive power equation is:

$$P_r = V_{\text{rms}} I_{\text{rms}}$$


The unit for reactive power is the VAR.

DT0082: Circuit 3 Devices 2 (ELTR-2001)
53

SCHOOL OF
ELECTRICAL AND
ELECTRONIC
ENGINEERING

Application of Inductors

Consider the case of two circuits connected with common lines as shown in Figure (a). A path for high frequency noise exists through the common grounds, creating a ground loop. The current in the ground can affect the signal. A special inductor, called a longitudinal choke is installed in the signal line. The ground loop sees a high impedance path, thus reducing the noise, while the low-frequency signal is coupled through the choke.

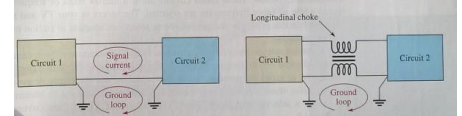

DT0082: Circuit 3 Devices 2 (ELTR-2001)
54

SCHOOL OF
ELECTRICAL AND
ELECTRONIC
ENGINEERING

Q of a coil - Figure of merit

In real Inductors the winding resistance appears as a resistance in series with the ideal inductor; it is referred to as DCR (DC resistance) or R_W . This resistance dissipates some of the reactive energy.

The **quality factor (Q)** of a coil is given by the ratio of reactive power to true power.

$$Q = \frac{I^2 X_L}{I^2 R_W}$$

For a series circuit, I cancels, leaving

$$Q = \frac{2\pi f L}{R_W}$$

DT0082: Circuit 3 Devices 2 (ELTR-2001)
55